



# 數位系統導論實驗 LAB 5

梁郁珮

2022/04/18

2022/04/20


# VHDL Modelling Styles

- Structure Description
- Dataflow Description
- Behavior Description


```
module LAB(clk, inA, inB, inC, outY, outX, outZ);  
  //-----Input ports-----  
  input  clk, inA, inB, inC;  
  //-----Structure-----  
  output [1:0]outX;  
  FA  x0(.A(inA), .B(inB), .Cin(inC), .S(outX[0]), .Cout(outX[1]));
```

```
  //-----Dataflow -----  
  output [1:0]outY;  
  assign outY = inA + inB + inC;
```

 
```
  //-----Behavior -----  
  output [1:0]outZ;  
  always@(posedge clk)  
  begin  
    outZ = inA + inB + inC;  
  end  
endmodule
```



← **FA**

 

# Sequential

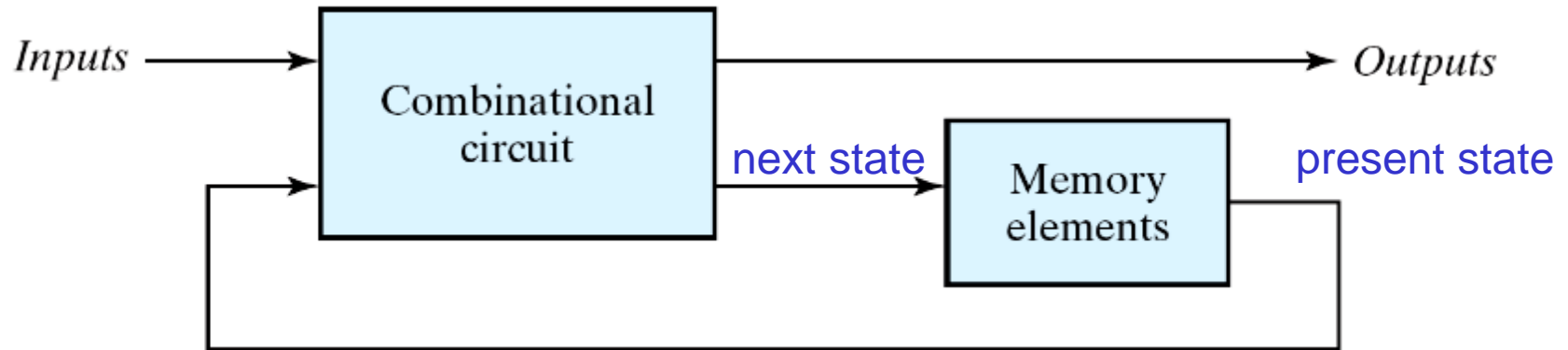


- A feedback path
- The state of the sequential circuit
- (inputs, current state)  $\Rightarrow$  (outputs, next state)
- **Synchronous**: the transition happens at discrete instants of time
- **Asynchronous**: at any instant of time



# SR latch

NOR:

'0' if either of its inputs are '1'

 


When a NOR has one input at '0', it inverts the other input

S = set  
R = reset  
Q = output

S	R	Q	Qb
1	0	1	0
0	1	0	1
0	0	hold	hold
1	1	0	0

When  
S and R  
are 0

 


國立中正大學

National Chung Cheng University



# SR latch type

 


(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)

(b) Function table

**FIGURE 5.3**

SR latch with NOR gates

 

(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1 (forbidden)

(b) Function table


**FIGURE 5.4**

SR latch with NAND gates





# SR latch w control

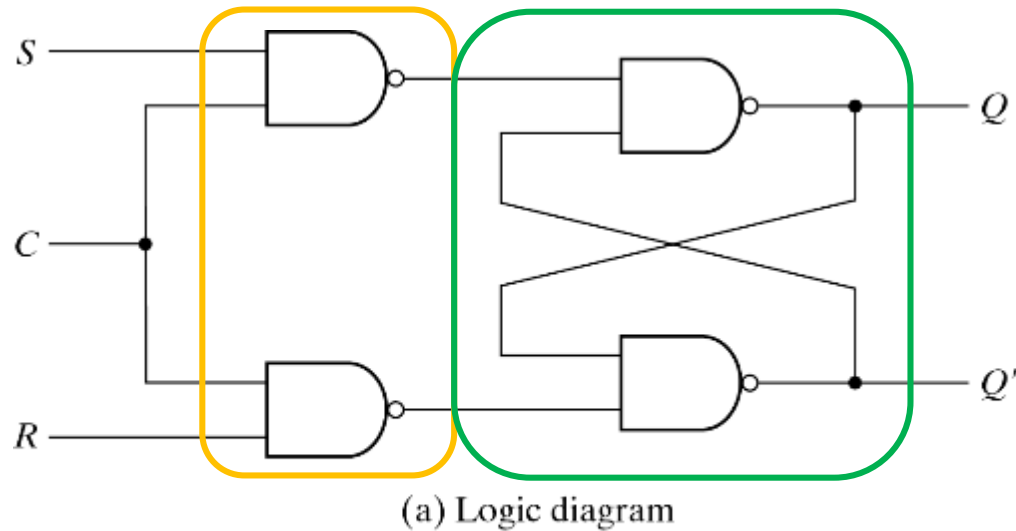

$C$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate


(b) Function table

Fig. 5-5 SR Latch with Control Input


- Occasionally, desirable to avoid latch changes
- $C = 0$  disables all latch state changes
- Control signal enables data change when  $C = 1$
- Right side of circuit same as ordinary S-R latch.




# D-Latch

 

(a) Circuit

 


(b) Graphical symbol

 


(c) Timing diagram




# Master-Slave D Flip Flop (neg.)

 

(a) Circuit

 

(b) Graphical symbol

 

(c) Timing diagram





# Master-Slave D Flip Flop (pos.)

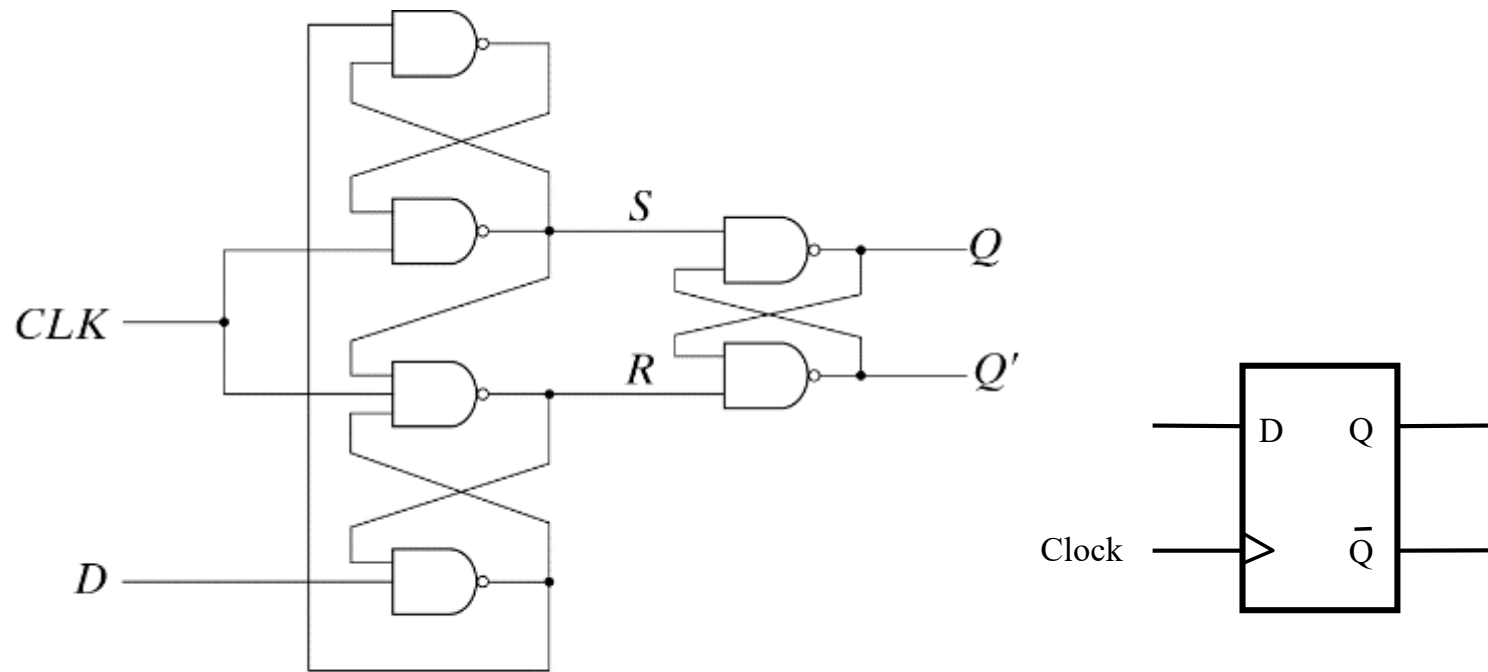


Fig. 5-10 D-Type Positive-Edge-Triggered Flip-Flop



# Latch & Flip-Flop

The state of a latch or flip-flop is switched by a change of the control input

- ◆ Level triggered – latches
- ◆ Edge triggered – flip-flops



(a) Response to positive level



(b) Positive-edge response




(c) Negative-edge response


Fig. 5-8 Clock Response in Latch and Flip-Flop



# Waveform

 

(a) Circuit

 

(b) Timing diagram



# Lexical conventions

Number format:

- Sized: default size is 32-bits decimal number

<bit length> ' <base><value>

reg d = 4'b1010 ; // sized constant

reg d = 4'd7 ; // sized constant

bit length	the length of desired value in bits.
base	It can be <b>b</b> (binary), <b>o</b> (octal), <b>d</b> (decimal) or <b>h</b> (hexadecimal)
value	It is any legal number in the selected based

- Unsized: default size is 32-bits

reg d = 7; // unsized constant, output bit length=32

reg [11:0]a;

a <= a + 1;

```
10230 Verilog HDL assignment warning at L277_Encoder.v(358): truncated value with size 32 to match size of target (12)
10230 Verilog HDL assignment warning at L277_Encoder.v(380): truncated value with size 32 to match size of target (12)
10230 Verilog HDL assignment warning at L277_Encoder.v(402): truncated value with size 32 to match size of target (12)
10230 Verilog HDL assignment warning at L277_Encoder.v(424): truncated value with size 32 to match size of target (12)
10230 Verilog HDL assignment warning at L277_Encoder.v(446): truncated value with size 32 to match size of target (12)
10230 Verilog HDL assignment warning at L277_Encoder.v(468): truncated value with size 32 to match size of target (12)
10230 Verilog HDL assignment warning at L277_Encoder.v(490): truncated value with size 32 to match size of target (12)
```



國立中正大學

National Chung Cheng University



# Lexical conventions(附錄)

Logical operators	
a && b	evaluates to true if a <i>and</i> b are true
a    b	evaluates to true if a <i>or</i> b are true
!a	converts non-zero value to zero, and vice versa

Shift operators	
a >> n a << n	logical shift right (left) n bit
a >>> n a <<< n	arithmetic shift right (left) n bit

Arithmetic operators	
a + b	a plus b
a - b	a minus b
a * b	a multiplied by b
a / b	a divided by b
a % b	a modulo b
a ** b	a to the power of b

Relational operators	
a < b	a less than b
a > b	a greater than b
a <= b	a less than or equal to b
a >= b	a greater than or equal to b

Bitwise operators	
a & b	a <i>and</i> b
a   b	a <i>or</i> b

Equality operators	
a === b	a equal to b, including x and z
a !== b	a not equal to b, including x and z
a == b	a equal to b, result can be unknown
a != b	a not equal to b, result can be unknown

請同學自行參考 ~




# Data assignment

## • Blocking assignment


- Evaluated and assigned in a single step
- Execution flow within the procedure is blocked until the assignment is completed

```
reg b, c;  
always@(posedge clk)  
begin  
    b = a;  
    c = b;  
end
```

Wrong

 

 register b has been combined and equivalent to c in the data behavior.




## • Non-Blocking assignment

- Evaluated and assigned in two steps
  - The right-hand side is evaluated immediately
  - The assignment to the left hand side is postponed until other evaluations in the current time step are completed


```
reg b, c;  
always@(posedge clk)  
begin  
    b <= a;  
    c <= b;  
end
```

Correct

 

Data can be passed sequentially from register b to c

 **SWAP**  
always @(posedge clk )  
begin  
 A <= B;  
 B <= A;  
end



Data Shift!!



國立中正大學

National Chung Cheng University





# Conditional Statement

```
if (<expression>
    <statement>
else if (<expression>
    <statement>
else if (<expression>
    <statement>
else (<expression>
    <statement>
```

```
if(cond[3])
    out=0
else if(!cond[3] & cond[2])
    out=1
else if(!cond[3] & !cond[2] & cond[1])
    out=2
else if(!cond[3] & !cond[2] & !cond[1] & cond[0])
    out=3
else if(!cond[3] & !cond[2] & !cond[1] & !cond[0])
    out=4
```


```
case (<expression>
    alternative1: <statement>
    alternative2: <statement>
    alternative3: <statement>
    .....
    .....
    default: <default statement>
endcase
```

```
case (cond.)
    4'b1???:
        out=0
    4'b01??:
        out=1
    4'b001?:
        out=2
    4'b0001:
        out=3
    4'b0000:
        out=4
endcase
```



 
# 實驗項目

- ◆ 使用內建50MHz時脈練習顯示「閃爍」CSIE 於A，時間間隔為1s亮一下



A




 

# REPORT OF LAB 5 (4%)

The report should include ...

 1. 完成下表
2. 在conditional statement中，若把if的條件式交換順序，答案還會一樣嗎？為什麼？
3. 心得與討論
4. 題目難度: 超難/難/普/易/超易



- File type: pdf
- File name: Lab5\_(Number of team)\_report
- Deadline: 2022/04/27 23:59

