



數位系統導論實驗 LAB 2

梁郁珮



1-BIT HALF ADDER (HA)

- Only can do **one-bit** addition


- Addition (1-bit)

- $0 + 0 = 00$
- $0 + 1 = 01$
- $1 + 0 = 01$
- $1 + 1 = 10$

x	Y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$C = XY$$

$$S = X'Y + XY' = X \oplus Y$$

 


How to add more bit?

- $A = (A_3A_2A_1A_0)$, $B = (B_3B_2B_1B_0)$
- $A + B$

$$\begin{array}{r} \\ \\ +) \\ \hline \end{array}$$

 Example:

$$\begin{array}{r} \\ \\ +) \\ \hline \end{array}$$



Full adder



- three input bits
 - x, y : two significant bits
 - Z (C_{in}): the carry bit from the previous lower significant bit
- Two output bits: C (C_{out}), S

x	y	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$
  
$$C = x'yz + xy'z + xyz' + xyz \\ = xy + xz + yz$$





IC介紹(74LS08) 4 * TWO-INPUT AND GATE

 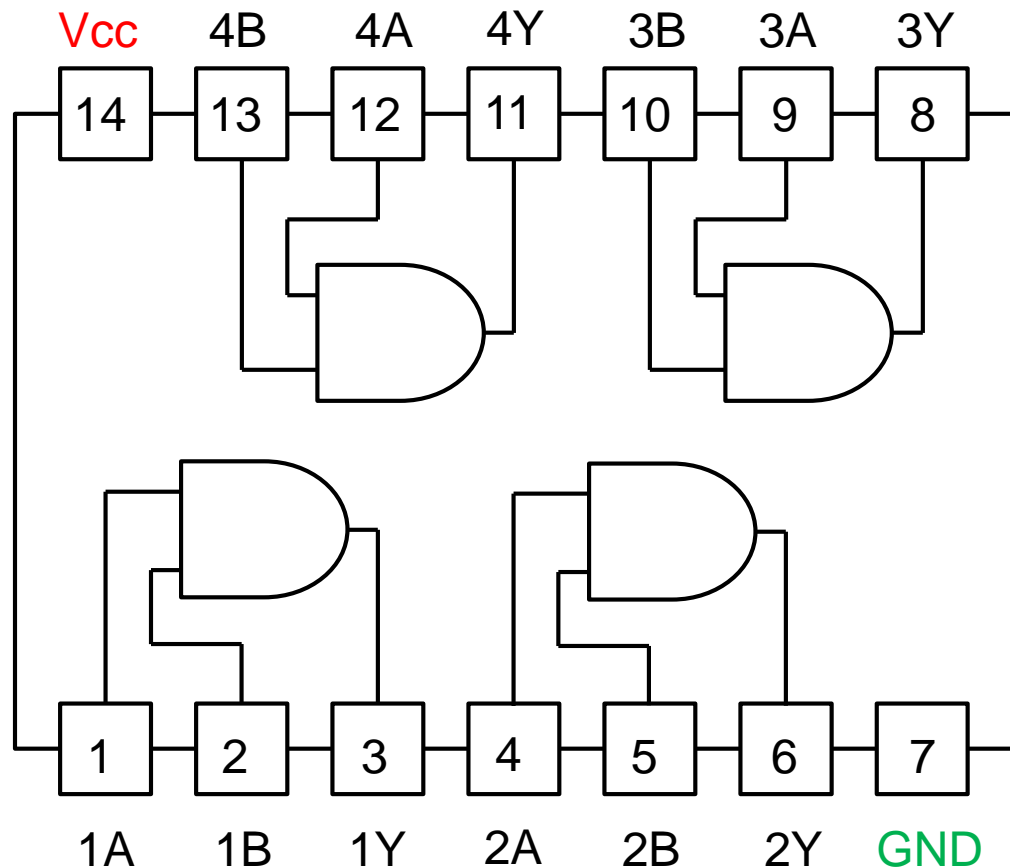



- 7及14接腳：接地及電源
- 1與2；4與5；9與10；12與13接腳：輸入腳位
- 3；6；8；11接腳：輸出腳位

IC介紹(74LS32) 4 * TWO-INPUT OR GATE

 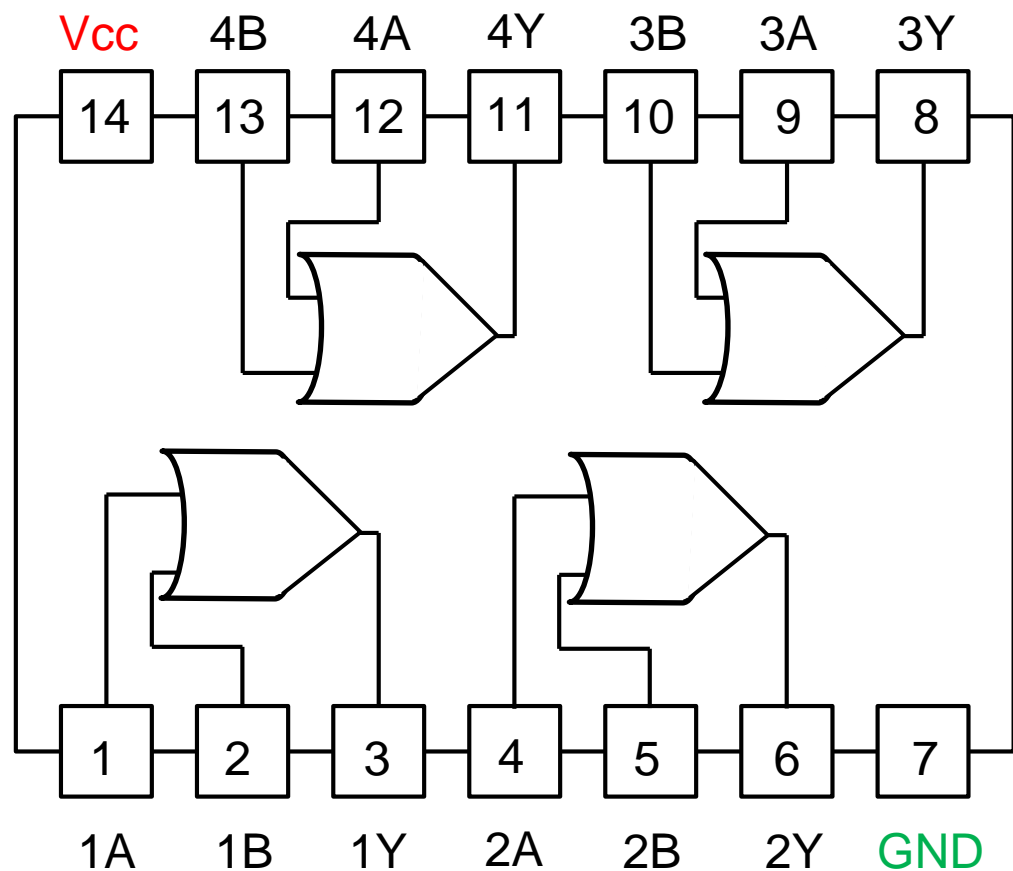



- 7及14接腳：接地及電源
- 1與2；4與5；9與10；12與13接腳：輸入腳位
- 3；6；8；11接腳：輸出腳位

IC介紹(74LS04) 6 * NOT GATE

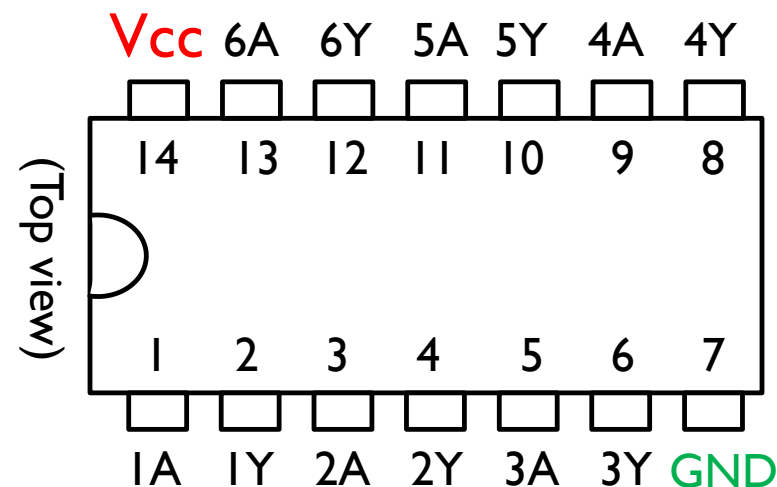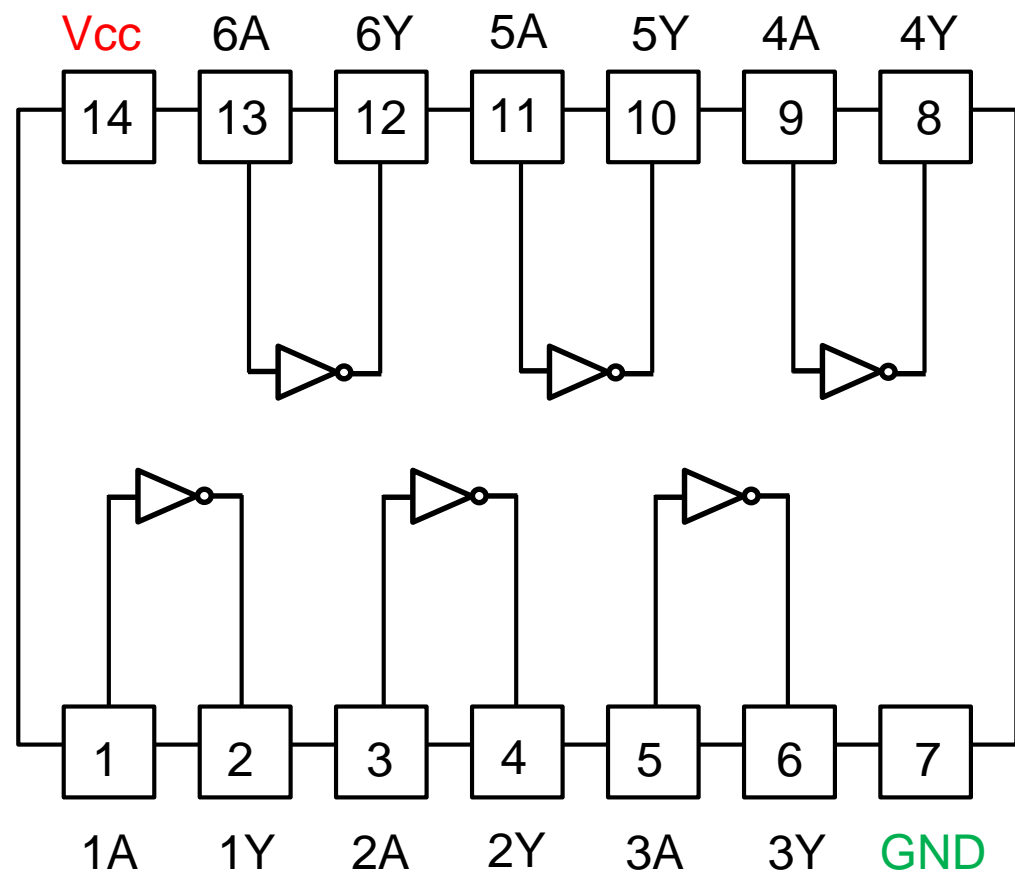



- 7及14接腳：接地及電源
- 1 ; 3 ; 5 ; 9 ; 11 ; 13 接腳：輸入腳位
- 2 ; 4 ; 6 ; 8 ; 10 ; 12 接腳：輸出腳位

IC介紹(74LS00) 4 * TWO-INPUT NAND GATE

 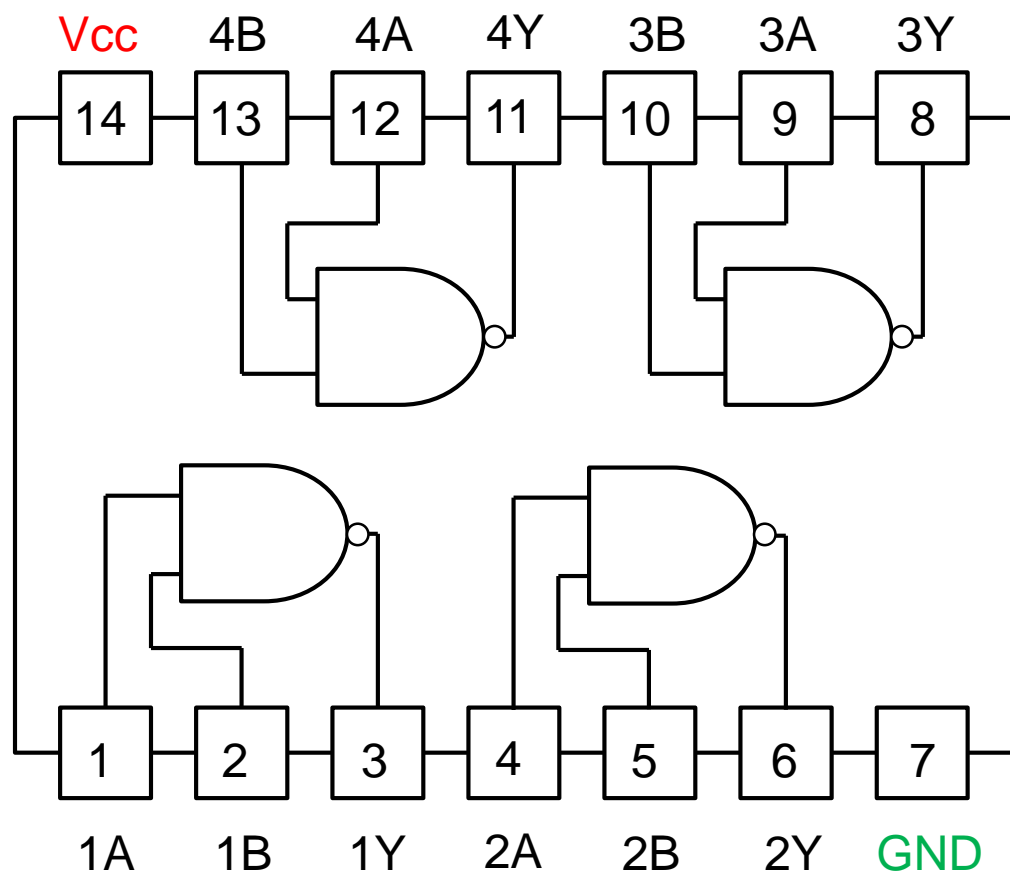

- 7及14接腳：接地及電源
- 1與2；4與5；9與10；12與13接腳：輸入腳位
- 3；6；8；11接腳：輸出腳位

IC介紹(74LS86) 4 * TWO-INPUT XOR GATE

 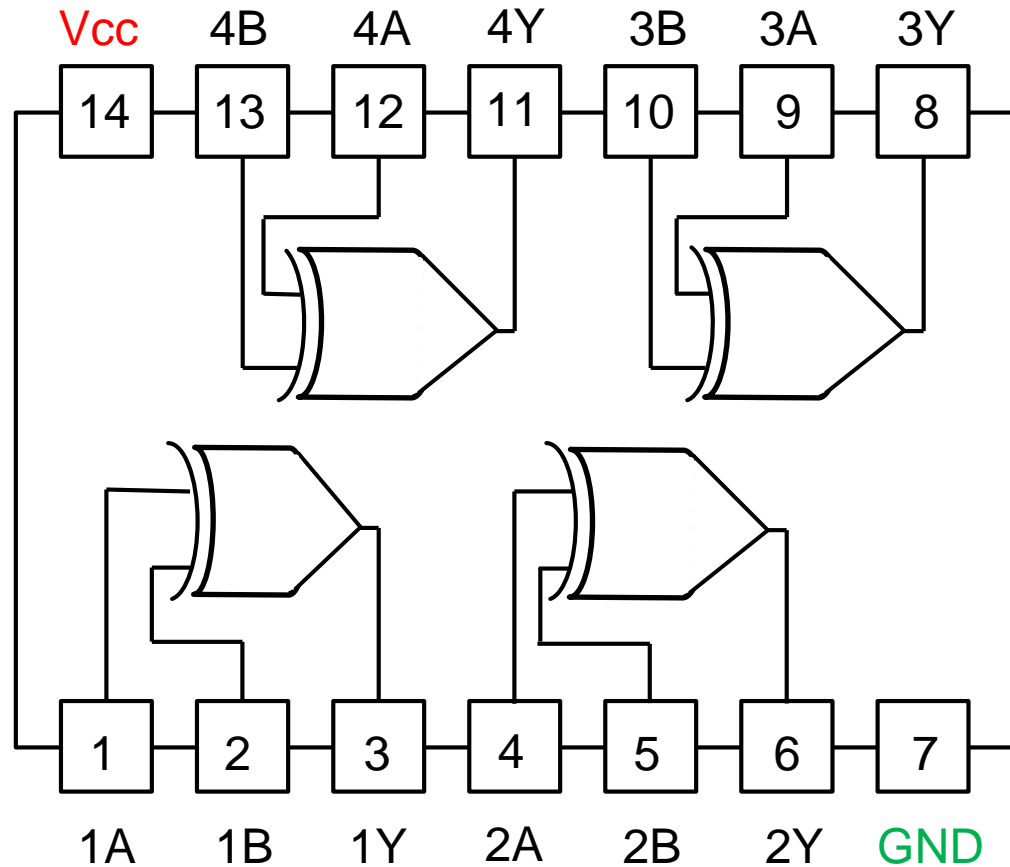


- 7及14接腳：接地及電源
- 1與2；4與5；9與10；12與13接腳：輸入腳位
- 3；6；8；11接腳：輸出腳位

• Lab 2-1 Implementing a full adder

1. Please implement a full adder with the following circuit

74LS08 (AND), 74LS32(OR), 74LS86(XOR)

 

實驗注意事項

1. 調整任何電路前請先將電源輸出關閉(output關掉, 輸入端線路移除, DC電源供應器power關掉 ...)，待電路調整完再開啟
2. 電源供應器需調整成 c.v. 模式，請注意c.v.燈號是否亮著
3. 輸入電壓固定為5V (請勿使用其他電壓)
4. 記得給IC正確的工作電壓 (腳位7, 14記得接地跟5V)

REPORT OF LAB 2 (4%)

The report should include ...

1. Discuss why the circuit on P.11 equals to the results on P.5
(討論P.11 與 P.5的電路為什麼相等)
 2. Draw logic diagrams to implement a full subtractor, and write the design procedures and Boolean equations for the implementations
(畫出以AND, OR, NOT, XOR實作全減器之接線圖，以及寫出設計過程及其布林函數)
 3. Discussion and experience (everyone)
(所有人的心得與討論)
- File type: pdf
 - File name: Lab2_(Number of team)_report
 - Deadline: 2022/3/28 24:00