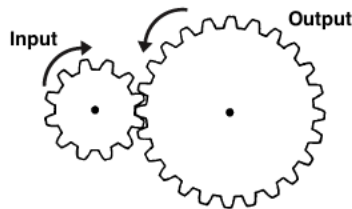


For each of the following digital designs, please

- (a) Construct its truth table;
 - (b) Show the minterm & maxterm expansions respectively;
 - (c) Show the equations of the simplified SoP & PoS respectively;
 - (d) Draw the simplified 2-level full-NAND and full NOR implementations respectively.
1. A design that outputs logic “1” iff the corresponding decimal of its 4-bit binary input $\{x_3 x_2 x_1 x_0\}$ is prime
 2. A design that outputs logic “1” iff the corresponding decimal of its 4-bit binary input $\{x_3 x_2 x_1 x_0\}$ is a Fibonacci number
 3. A design that converts a 4-bit binary number to its Gray code
 4. A design that derives the output gear count from a 4-bit counter for the input gear (the ratio of two gears is 5:1)



5. A design that sums up its 4 binary inputs a, b, c , and d (i.e., $\{y_2 y_1 y_0\} = a+b+c+d$)
6. A design that multiplies its two 2-bit inputs (both the inputs and output are signed numbers with the 2's complement representation)